

Digital Cash Register: Report

THEORY:

The main idea behind our *digital cash register* project is really simple. Our project circuit consists of four main parts. They are the *Card Identification System*, the *Memory Unit*, the *Counting System* and the *Display System*. The *Card Identification System* identifies the product that the buyer wants to buy using a specific '**Product Card**' and *IR Emitters & IR Receivers*. The *Memory Unit* preserves the prices of all the goods offered. The *Counting System* consists of two types of counting systems — *Binary Down-counting* and *BCD Up-counting System*. The *Binary* counter down-counts from the product's price to zero one after another, effectively summing up the prices. Switches are used to control *data loading* and *counting*. Finally, the *Display System* shows the results of addition in *BCD* format.

INSTRUMENTS USED:

- ✂ *Timer ICs* — IC **555**
- ✂ *Quad Op-Amps* — IC **LM324**
- ✂ *16 to 1 Multiplexers* — IC **74150**
- ✂ *4 Bit Binary Up/Down Counters* — IC **74191**
- ✂ *BCD Up/Down Counters* — IC **74190**
- ✂ *Logical OR Gate ICs* — IC **7432**
- ✂ *NOT Gate ICs* — IC **7404**
- ✂ *Infrared Emitters & Infrared Receivers*
- ✂ *5 V Power Supply Regulator ICs* — IC **7805** & corresponding **Heat Sink**
- ✂ *7 Segment Displays & corresponding Display Driver ICs* — IC **7447**
- ✂ *Resistors, Potentiometers, Capacitors & LEDs*
- ✂ *12 V Adapter & SPDT Switches*
- ✂ *Breadboards & Connecting Wires*

OPERATION:

The operation of our circuit is quite interesting. The *cash register* works by **identifying** the products & corresponding prices, **summing up** them as well as **displaying** it to both the seller and the buyer. The operation of the circuit can be divided into *four steps*. So, here's the steps —

First, Card Identification System

The identification of a product leads to finding out the price of that specific product. To implement this, we have used a *Card Identification System*. We have kept a '**Product Card**' for each product holding a specific ID Number (in *Binary* format) of the corresponding product. To read this number, we have used a **Sensor/Reader Circuit** consisting of *Infrared Emitters* and *Infrared Receivers* placed *face-to-face*. The card is inserted between them. The circuit reads **1** when the infrared ray is received and **0** when it is blocked and so these cards have 4 **bars** for 4 *Bit data* which are either *empty* (read as **1**) or *solid* (read as **0**).

Second, Memory Unit

We have implemented this unit using four *16 to 1 Multiplexer ICs* (IC **74150**). So, there is a highest of 16 products that can be identified. Also, the highest price that can be set is **15 units** (in *binary 1111*, i.e., *highest number in 4 Bit data system*). By adding more Bits, the number of products and the highest price

can be extended up to the choice). The ID No. read in the *Reader* is sent to the *common selector* pins of the *MUXs*. This enables a special number of input pin in each *MUX* which holds the product's price to send it to the output pin.

Third, Counting System

The *Counting System* for sums up the prices of all the products that a buyer buys to the total. The *Counting System* is consists of two types of counting —

➤ Binary Down-counting —

We have implemented this using one *IC 74191* which is a *4 Bit Binary Up/Down Counter*. It is used as a *Down-Counter* only by making the *D/U* pin (pin 5) = **1**. The price of a product in *4 Bit data* from the *MUX* output pins is sent to the inputs of this counter. Then, the counter *down-counts* from that price to zero.

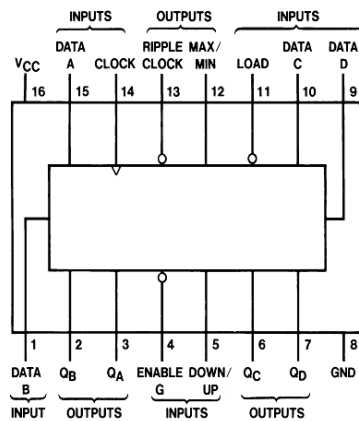


Fig: Pin diagram of *IC 74191*

➤ BCD Up-counting —

We have implemented this using two *IC 74190's* which are *BCD Up/Down Counters*. It is used as an *Up-Counter* only by making the *D/U* pin (pin 5) = **0**. When the *Binary* counter *down-counts*, the *BCD* counter block *up-counts* from zero to the product's price simultaneously and stays there until it is manually cleared.

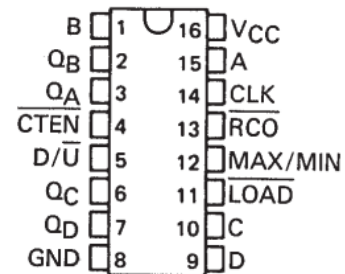


Fig: Pin diagram of *IC 74190*

If a second price comes to next, the *BCD* counter block counts from the previous point (1st product's price) to the sum of the two prices, effectively *adding* the prices. Similarly, more prices can be added. Thus, the *Counting System* sums up the prices of all the products that a buyer buys.

The *Binary* counter is the core unit here, as price *data* is loaded into it for counting. There are several switches to control the *adding* process —

☐ LOAD/COUNT Switch —

This switch controls the *loading* of price to the *Counting System* and the counting. When *LOAD/COUNT* = **1**, the price *data* is loaded into the *Binary* counter and when *LOAD/COUNT* = **0**, the counters count.

☐ MASTER RESET Switch —


This switch is needed when more than one buyer comes into account. After one buyer's prices are

summed up to total, pushing this switch starts counting from zero again. *MASTER RESET* Switch is implemented by simply connecting the *LOAD* pins (pin 11) to a switch.

When the *BCD* counter reaches to the price and *Binary* counter reaches to zero, the *MAX/MIN* pin of *Binary* counter (pin 12) changes to **1** from **0** which makes the *Common Enabler* of the *Counting System* 1. As the counter ICs are *active low*, they stop counting. By varying the *Clock frequency*, the counting can be made of certain speed.

Fourth, Display System

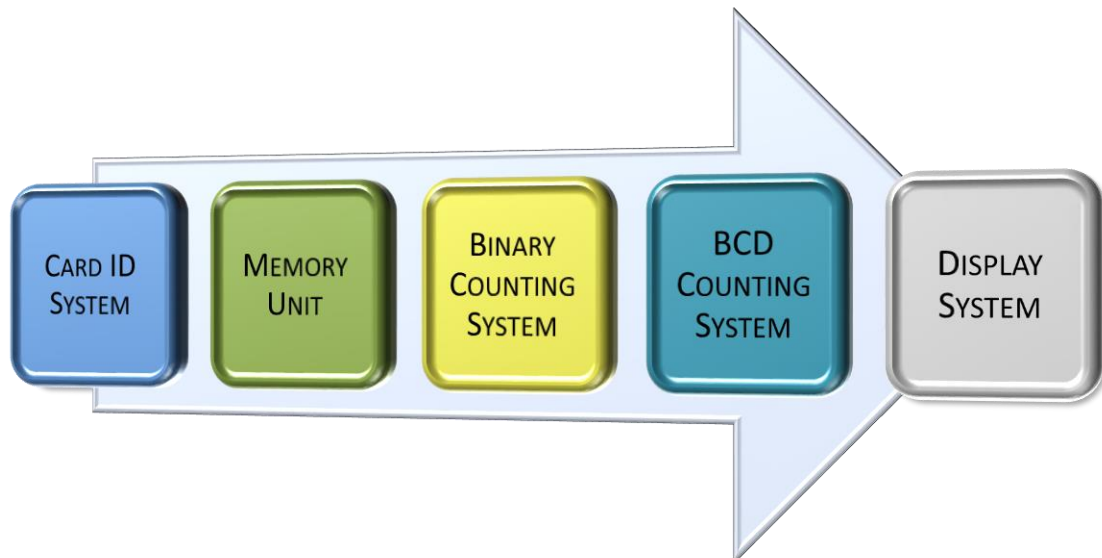The *Display System* shows the results of addition. We have implemented the *Display System* using *7 Segment Displays*. There is two *7 Segment Displays* for two *BCD* counter driven by two *Display Driver* ICs (*IC 7447*). Here, the largest sum that can be displayed is **99**.



Digital Cash Register System Flow Chart

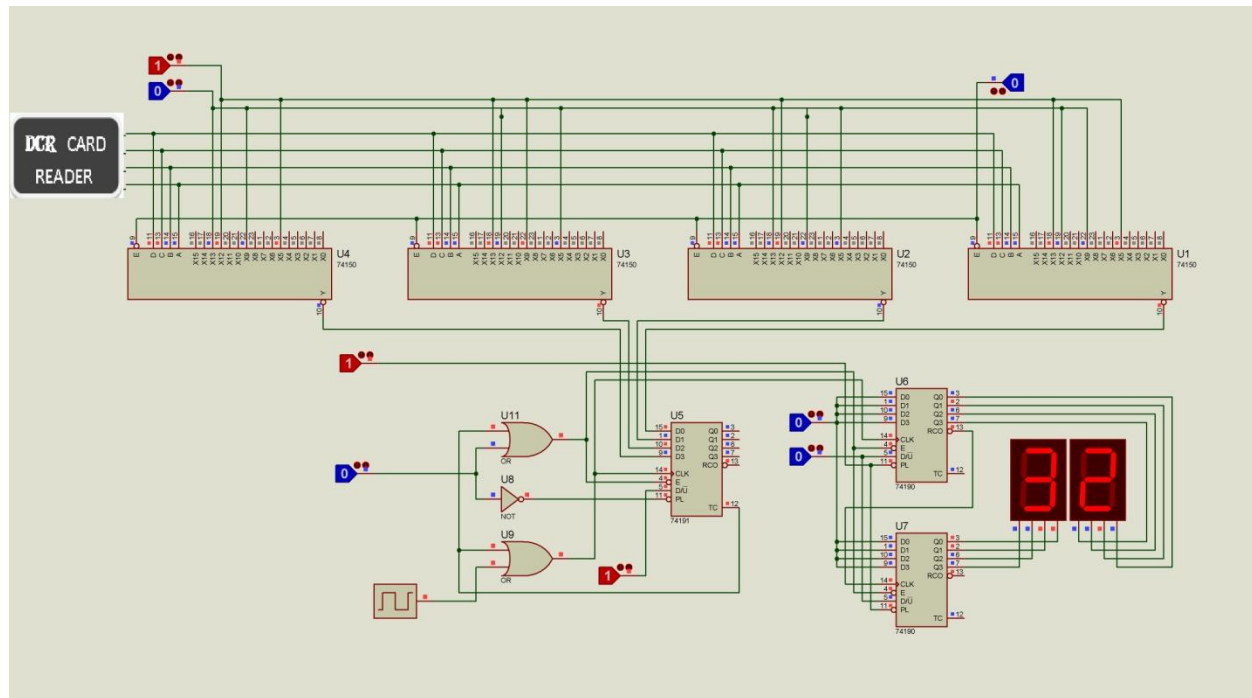
CIRCUIT DIAGRAM:

Fig: Digital Cash Register System
